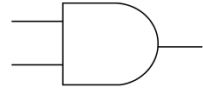
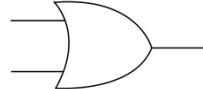
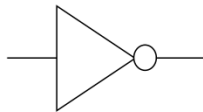


2.4.1 Boolean logic

- ☐ Simple logic diagrams using the operators AND, OR and NOT
- ☐ Truth tables
- ☐ Combining Boolean operators using AND, OR and NOT
- ☐ Applying logical operators in truth tables to solve problems

Required

- ✓ Knowledge of the truth tables for each logic gate
- ✓ Recognition of each gate symbol
- ✓ Understanding of how to create, complete or edit logic diagrams and truth tables for given scenarios
- ✓ Ability to work with more than one gate in a logic diagram

Boolean Operators	Logic Gate Symbol
AND (Conjunction)	
OR (Disjunction)	
NOT (Negation)	

Truth Tables

AND			OR			NOT	
A	B	A AND B	A	B	A OR B	A	NOT A
0	0	0	0	0	0	0	1
0	1	0	0	1	1	1	0
1	0	0	1	0	1		
1	1	1	1	1	1		

Alternatives

- Use of other valid notation will be accepted within the examination, e.g. Using T/F for 1/0, or V for OR, etc.